

Let's Build – Series 2


Let's build some useful IOT Projects

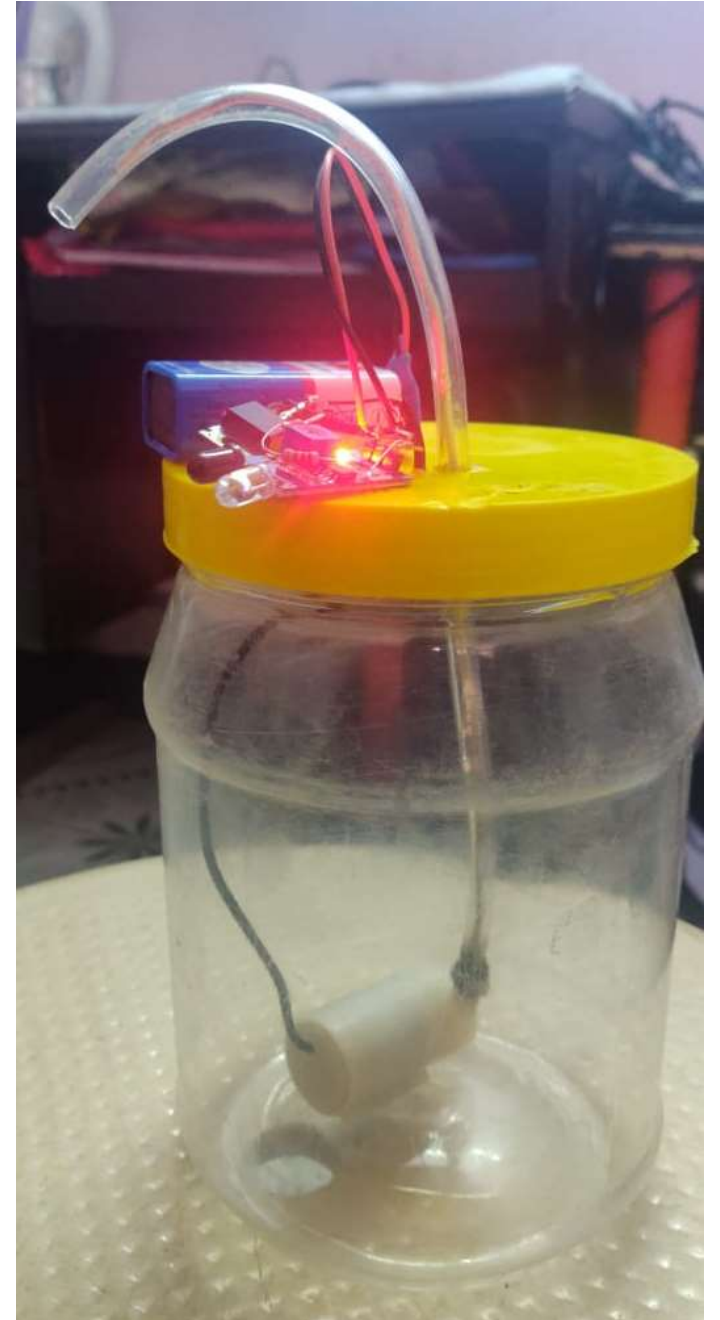1. Automatic Hand Sanitizer



Automatic Hand Sanitizer


Build the simplest Automated Alcohol Dispenser to keep your hands clean by filling it hand sanitizer.



Sensors & Tools used



Circuit Diagram

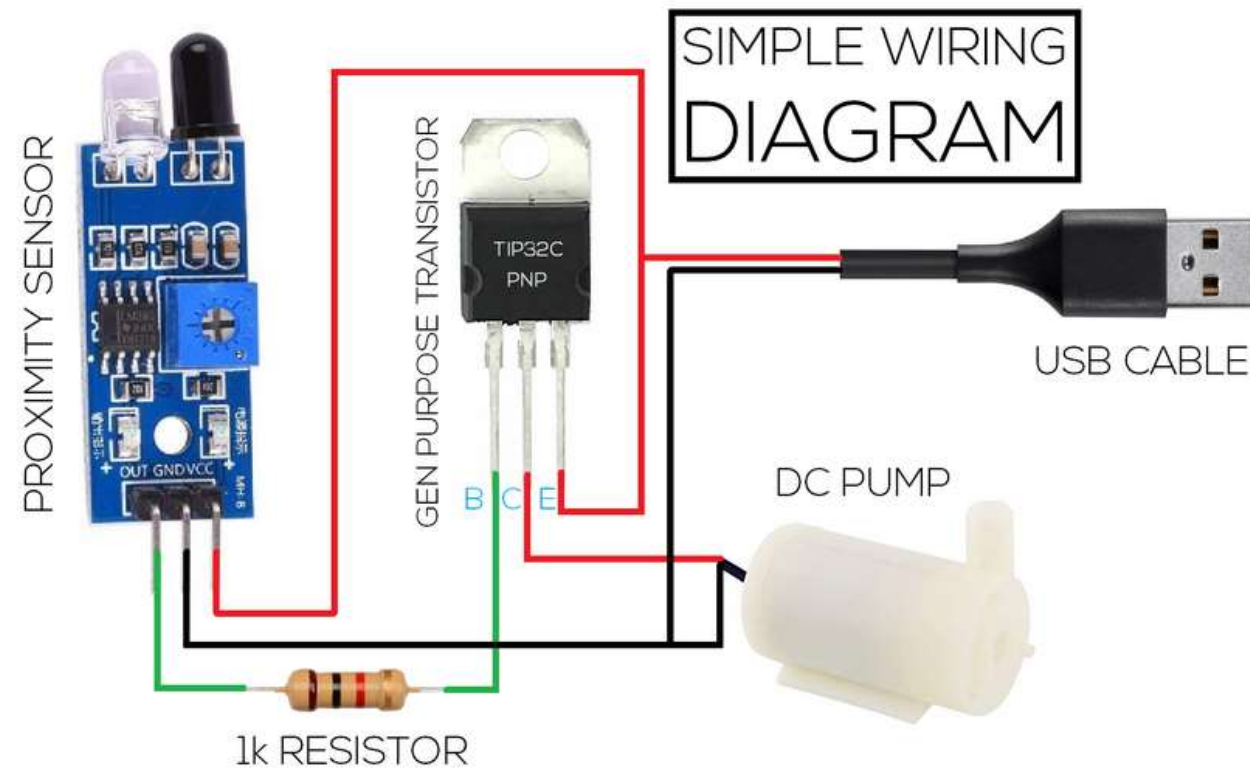

Working

- The IR sensor detects human hand interference.
- Then activates the DC Pump via the TIP32C Transistor.
- Hurrah 😊 Now your hands are clean.

Final Product

